

Practical No. 8

Aim: To implement 4-bit magnitude comparator.

Apparatus: 4 bit magnitude comparator IC (74LS85), Connecting wires, Bread Board, Power supply, LED, DMM.

Theory:

Definition

A magnitude comparator is a combinational circuit that compares two numbers **A** & **B** to determine whether:

- **A** > **B**, or
- **A** = **B**, or
- **A** < **B**

Inputs

First **n**-bit number **A**


Second **n**-bit number **B**

Outputs

3 output signals (GT, EQ, LT), where:

 1. **GT** = 1 IFF **A** > **B**
2. **EQ** = 1 IFF **A** = **B**
3. **LT** = 1 IFF **A** < **B**

Note: Exactly One of these 3 outputs equals 1, while the other 2 outputs are 0's



4-bit magnitude comparator

Inputs: 8-bits (**A** ⇒ 4-bits, **B** ⇒ 4-bits)

A and **B** are two 4-bit numbers

- Let **A** = **A**_{3**A**_{2**A**_{1**A**₀, and}}}
- Let **B** = **B**_{3**B**_{2**B**_{1**B**₀}}}
- Inputs have 2⁸ (256) possible combinations
- Not easy to design using conventional techniques

Design of the EQ output ($A = B$) in 4-bit magnitude comparator

Define $X_i = (A_i B_i) + (A_i' B_i')$

Thus $X_i = 1$ IFF $A_i = B_i \quad \forall i = 0, 1, 2 \text{ and } 3$
 $X_i = 0$ IFF $A_i \neq B_i$

Condition for $A = B$

$EQ = 1$ (i.e., $A = B$) IFF

1. $A_3 = B_3 \rightarrow (X_3 = 1)$, and
2. $A_2 = B_2 \rightarrow (X_2 = 1)$, and
3. $A_1 = B_1 \rightarrow (X_1 = 1)$, and
4. $A_0 = B_0 \rightarrow (X_0 = 1)$.

Thus, $EQ = 1$ IFF $X_3 X_2 X_1 X_0 = 1$. In other words, $EQ = X_3 X_2 X_1 X_0$

Design of the GT output ($A > B$) 4-bit magnitude comparator

If $A_3 > B_3$, then $A > B$ ($GT = 1$) irrespective of the relative values of the other bits of A & B . Consider, for example, $A = 1000$ and $B = 0111$ where $A > B$.

This can be stated as $GT = 1$ if $A_3 B_3' = 1$

If $A_3 = B_3$ ($X_3 = 1$), we compare the next significant pair of bits (A_2 & B_2).

If $A_2 > B_2$ then $A > B$ ($GT = 1$) irrespective of the relative values of the other bits of A & B . Consider, for example, $A = 0100$ and $B = 0011$ where $A > B$.

This can be stated as $GT = 1$ if $X_3 A_2 B_2' = 1$

If $A_3 = B_3$ ($X_3 = 1$) and $A_2 = B_2$ ($X_2 = 1$), we compare the next significant pair of bits (A_1 & B_1).

If $A_1 > B_1$ then $A > B$ ($GT = 1$) irrespective of the relative values of the remaining bits A_0 & B_0 . Consider, for example, $A = 0010$ and $B = 0001$ where $A > B$

This can be stated as $GT = 1$ if $X_3 X_2 A_1 B_1' = 1$

If $A_3 = B_3$ ($X_3 = 1$) and $A_2 = B_2$ ($X_2 = 1$) and $A_1 = B_1$ ($X_1 = 1$), we compare the next pair of bits (A_0 & B_0).

If $A_0 > B_0$ then $A > B$ ($GT = 1$). This can be stated as $GT = 1$ if $X_3 X_2 X_1 A_0 B_0' = 1$

To summarize, $GT = 1$ ($A > B$) IFF:

1. $A_3 B_3' = 1$, or
2. $X_3 A_2 B_2' = 1$, or
3. $X_3 X_2 A_1 B_1' = 1$, or
4. $X_3 X_2 X_1 A_0 B_0' = 1$


In other words, $GT = A_3 B_3' + X_3 A_2 B_2' + X_3 X_2 A_1 B_1' + X_3 X_2 X_1 A_0 B_0'$

Design of the LT output ($A < B$) 4-bit magnitude comparator


In the same manner as above, we can derive the expression of the LT ($A < B$) output






$$LT = B_3 A_3' + X_3 B_2 A_2' + X_3 X_2 B_1 A_1' + X_3 X_2 X_1 B_0 A_0'$$

The gate implementation of the three output variables (EQ, GT & LT) is shown in the figure below.

 Logic Diagram:**Procedure:**

- Do the connection as per below pin diagram for various input data or 4 bit number.
- Apply proper input condition and observe the output information of led on/off.
- Compare theoretical data with observation and write conclusion.

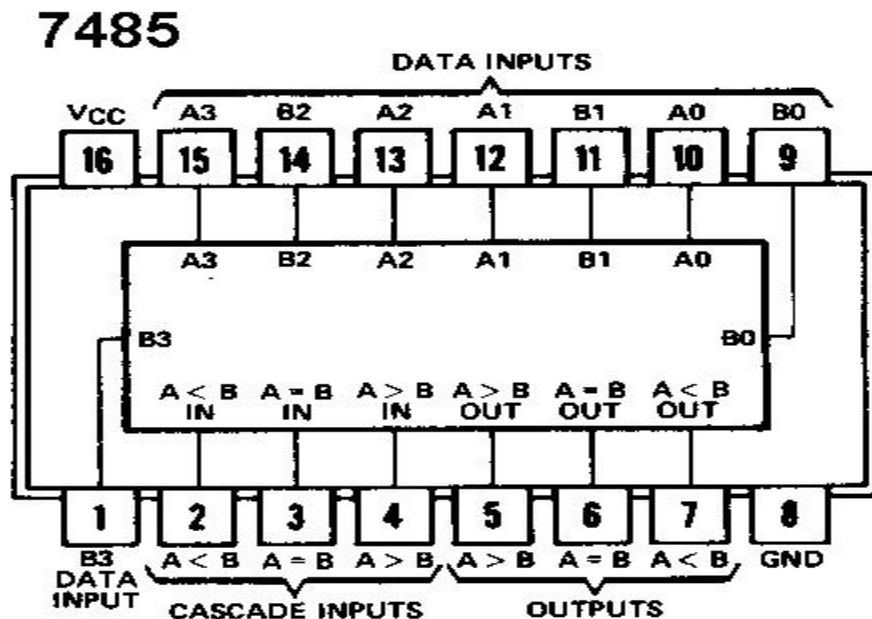Pin Diagram:

     


BCD to Excess-3 Code conversion logic diagram

Procedure:

- i) Do the connection as per Combinational logic diagram for various input data.
 - ii) Apply proper input condition and observe the output information of using DMM.
- Compare theoretical data with observation and write conclusion

Inputs					Outputs		
A ₁	A ₀	B ₁	B ₀		G	E	L
0	0	0	0		0	1	0
0	0	0	1		0	0	1
0	0	1	0		0	0	1
0	0	1	1		0	0	1
0	1	0	0		1	0	0
0	1	0	1		0	1	0
0	1	1	0		0	0	1
0	1	1	1		0	0	1
1	0	0	0		1	0	0
1	0	0	1		1	0	0
1	0	1	0		0	1	0
1	0	1	1		0	0	1
1	1	0	0		1	0	0
1	1	0	1		1	0	0
1	1	1	0		1	0	0
1	1	1	1		0	1	0

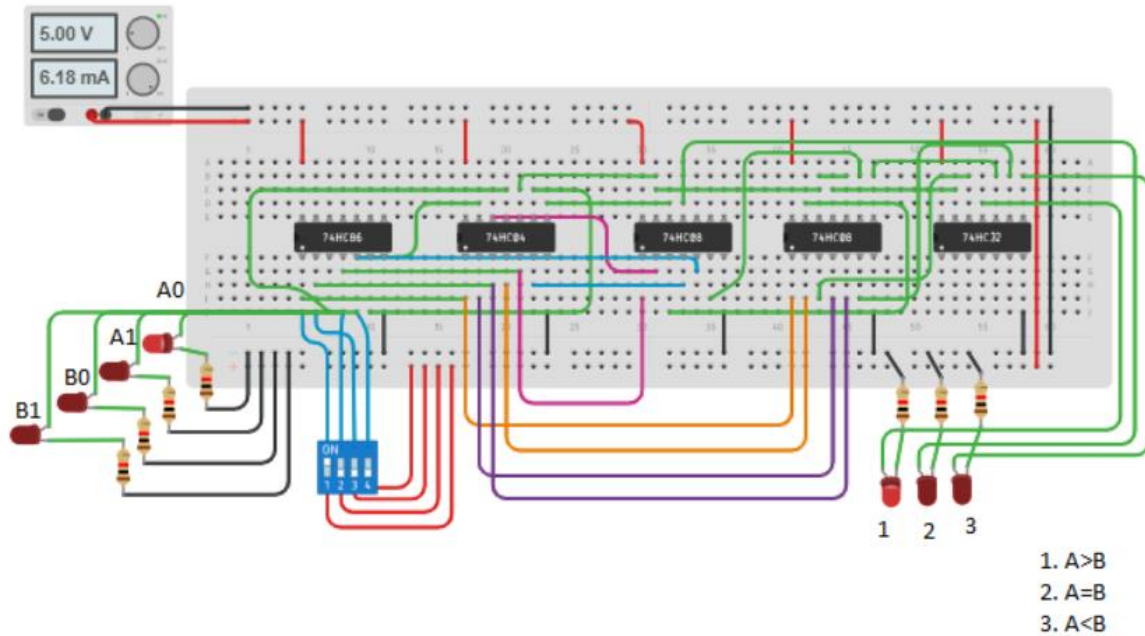CIRCUIT DIAGRAMS:**2- Bit Magnitude comparator****CONCLUSION:**

Comparators compares an input signal with a reference voltage and has as a result a logic stage, which indicates whether the signal is lower or higher.