

## Practical No. 7

**Aim: To perform BCD to Excess-3 conversion.**

**Apparatus:** Logic Gate ICs, Connecting wires, Bread Board, Power supply, LED, DMM.


### Theory:

We will complete this experiment to code converters by designing an Excess-3 Binary Coded Decimal (BCD) circuit. The term BCD refers to representing the ten decimal digits in binary forms; which simply means to count in binary; see Table below. The Excess-3 system simply adds 3 to each number to make the codes look different. We will not venture to discuss the importance of the Excess-3 BCD system because the discussion would serve too great a distraction from our present purpose and the cost would outweigh the benefit. Suffice it to say that the Excess-3 BCD system has some properties that made it useful in early computers.

The Excess-3 BCD system is formed by adding 0011 to each BCD value as in Table. For example, the decimal number 7, which is coded as 0111 in BCD, is coded as  $0111 + 0011 = 1010$  in Excess-3 BCD.

Decimal	BCD				Excess-3			
	8	4	2	1	BCD + 0011			
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

## Tinker Cad Simulation:

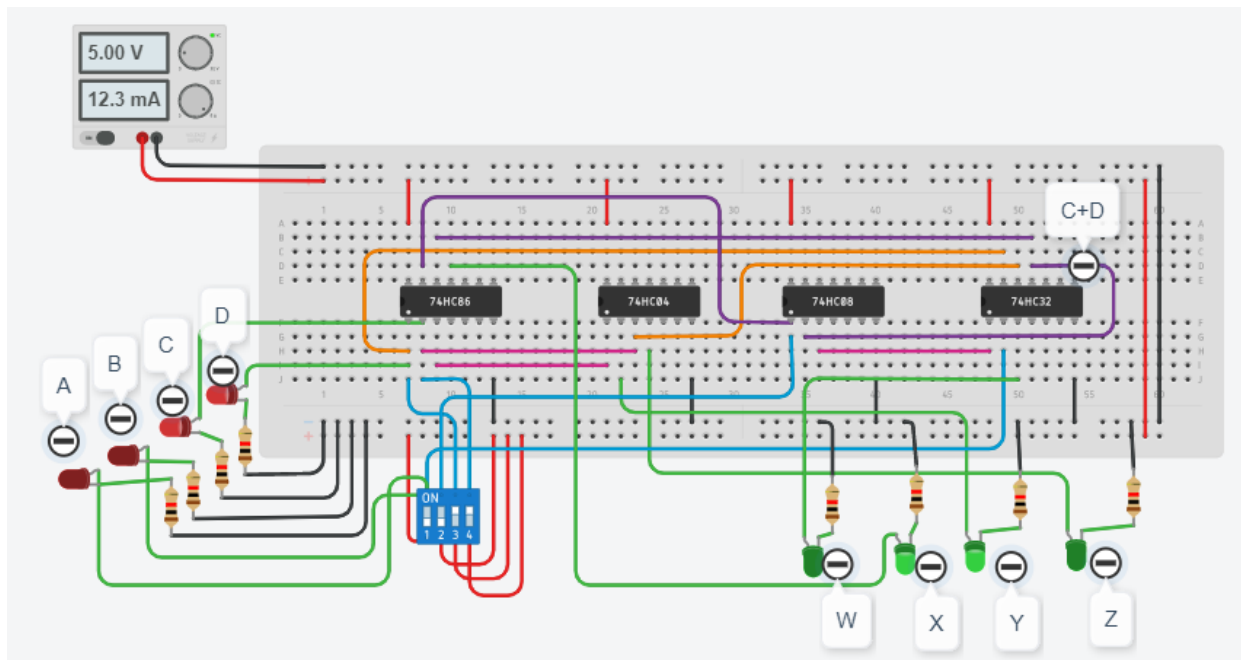

## CONCLUSION:

Excess-3 binary code is a unweighted self-complementary BCD code. Self-Complementary property means that the 1's complement of an excess-3 number is the excess-3 code of the 9's complement of the corresponding decimal number. This property is useful since a decimal number can be nines' complemented (for subtraction) as easily as a binary number can be ones' complemented; just by inverting all bits.