

Practical No. 1

Aim:

Study of logic gates (AND, OR, NOT, NAND, NOR, Ex-OR).

Apparatus:

connecting wires, power supply, bread board, ICs as follow


Sr. No.	Component	Specification	Quantity
1	AND Gate	IC 7408	1
2	OR Gate	IC 7432	1
3	NOT Gate	IC 7404	1
4	NAND Gate	IC 7400	1
5	NOR Gate	IC 7402	1
6	X-OR Gate	IC 7486	1

Theory:

Circuit that takes the logical decision and the process are called logic gates. Each gate has one or more input and only one output. OR, AND & NOT are basic gates. NAND, NOR, XOR are known as universal gates. Basic gates can be obtained from all this gate.

AND Gate:

The AND gate performs a logical multiplication commonly known as AND function. The output is high only when both the input are either one high or one low. When both the input are high the output is low level.

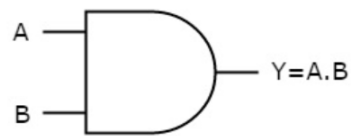
SYMBOL:**Observation Table:**

INPUT	INPUT	OUTPUT
0	0	0
0	1	0
1	0	0
1	1	1

OR Gate:

The OR gate performs a logical addition commonly known as OR function.

The output is high when any one of the inputs is high and the output is low level when both the inputs are low.

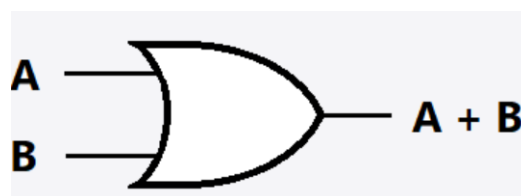
Symbol:

Observation Table:

INPUT	INPUT	OUTPUT
0	0	0
0	1	1
1	0	1
1	1	1

NOT Gate:


The NOT gate is called an inverter. The output is high when the input is low. The output is low when the input is high.

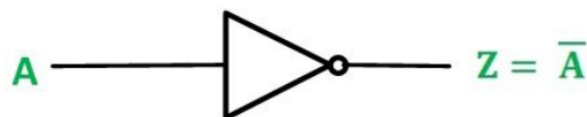Symbol:**Observation Table:**

INPUT	OUTPUT
0	1
1	0

NAND Gate:

The NAND gate is a contraction of AND-NOT. The output is high when both inputs are low and any one of the input is low. The output is low level when the input are high.

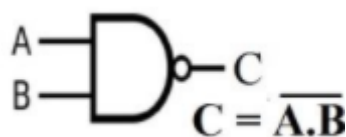
Symbol:

Observation Table:

INPUT	INPUT	OUTPUT
0	0	1
0	1	1
1	0	1
1	1	0

NOR Gate


The NOR gate is contraction of OR-NOT. The output is high when both inputs are low. The output is low when one or both inputs are high.

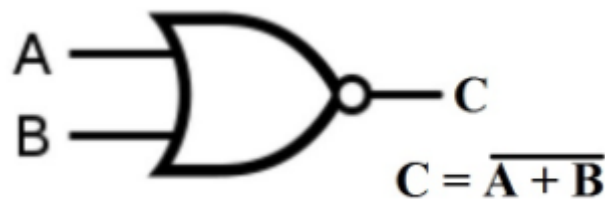Symbol:**Observation Table:**

INPUT	INPUT	OUTPUT
0	0	1
0	1	0
1	0	0
1	1	0

X-OR Gate:

The output is high when any one of the input is high. The output is also low when both the inputs are low and both inputs are high.

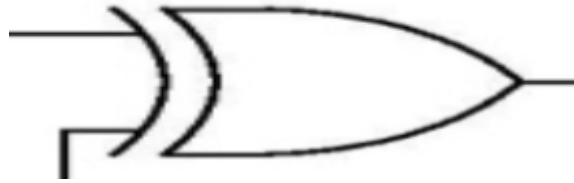Symbol:**OBSERVATION:**

INPUT	INPUT	OUTPUT
0	0	0
0	1	1
1	0	1
1	1	0

CONCLUSION:

By studying the above practical , we learned characteristics of many LOGIC gates of DIGITAL ELECTRONICS.