

## D.E Assignment - 2

(1) Demonstrate by means of truth table, validity of both Distributive Laws.

$$\rightarrow (.) \text{ over } (+) \rightarrow A, (B+C) = (A,B) + (A,C)$$

A	B	C	$B+C$	$A \cdot B$	$A \cdot C$	$(A \cdot B) + (A \cdot C)$	$A \cdot (B+C)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	0	1	1	1
1	1	1	1	1	1	1	1
1	1	0	1	1	0	1	1

$$\Rightarrow (+) \text{ over } \text{or} \text{ or } \rightarrow A + (B \cdot C) = (A+B) \cdot (A+C)$$

19DCS092

(2)

(2) Simplify the Boolean functions to minimum literals :-

$$\begin{aligned}
 \text{(a)} \quad & (x+y)(x+y') = x \cdot x + x \cdot y' + y \cdot x + y \cdot y' \\
 & = x + x \cdot y' + x \cdot y + 0 \\
 & = x + x(y' + y) \\
 & = x + x \\
 & = \underline{\underline{x}}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b)} \quad & xyz + x'y + xy'z' = y \cdot (xz + x' + xz') \\
 & = y \cdot \{ x' + x(z+z') \} \\
 & = y \cdot \{ x' + x \} \\
 & = y \\
 & = \underline{\underline{y}}
 \end{aligned}$$


$$\begin{aligned}
 \text{(c)} \quad & xz + x'y z = z \cdot (x + x'y) \\
 & = z \cdot [(x+x') \cdot (x+y)] \\
 & = z \cdot (x+y) \\
 & = z \cdot x + z \cdot y \\
 & = \underline{\underline{z \cdot x + z \cdot y}}
 \end{aligned}$$

$$\begin{aligned}
 \text{(d)} \quad & (a+b)'(a'+b')' = a'b' \cdot (a, b) \\
 & = a \cdot a' \cdot b \cdot b' \\
 & = 0 \cdot 0 = 0
 \end{aligned}$$

$$\begin{aligned}
 \text{(e)} \quad & y(wz' + wz) + xy = y[w \cdot (z+z')] + xy \\
 & = y \cdot w + \underline{\underline{x \cdot y}} \\
 & = \underline{\underline{y \cdot (w+x) + xy}}
 \end{aligned}$$

(3) For given:-  $F = XY + X'Y' + Y'Z$

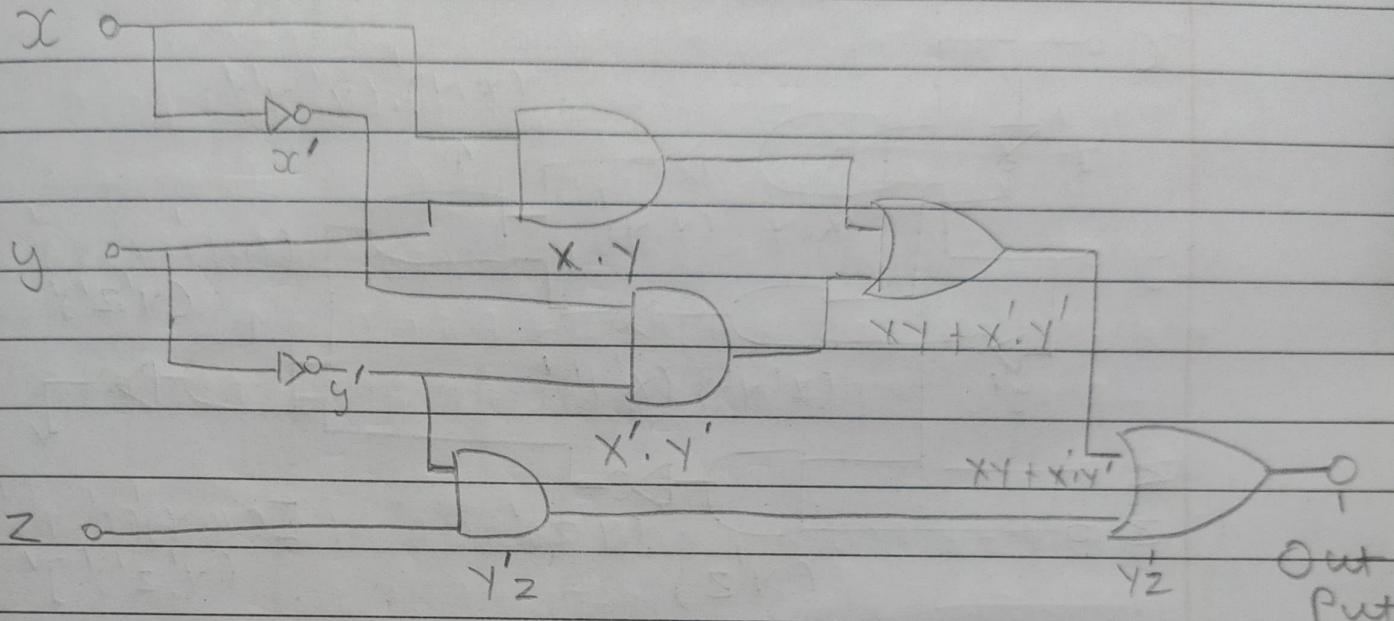
(1) Implement using (3) AND, (2) OR, (2) NOT gates



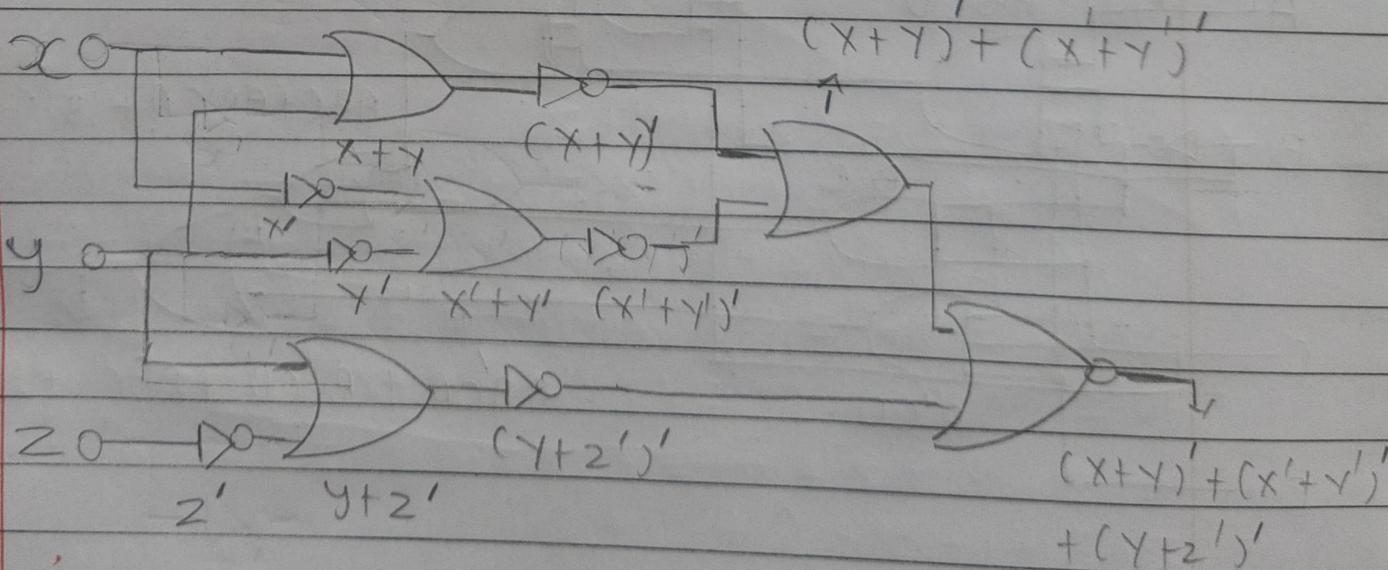(2) Implement using 5(OR) and 6(NOT) gates

$$F = XY + X'Y' + Y'Z$$


→ Using De Morgan's law  $\Rightarrow F = (X' + Y')' + (X + Y)' + (Y + Z')'$



(3) Implement with (5) AND and (8) NOT gates

$$F = XY + X'Y' + Y'Z$$


$$F = [(XY)'(X'Y')'(Y'Z)']'$$

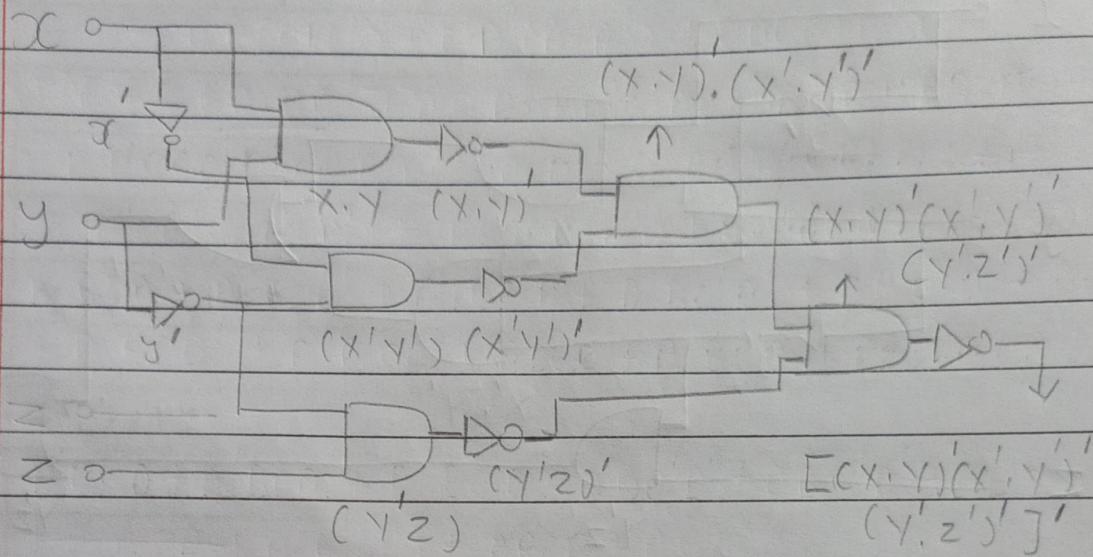

Q-4

Draw the circuit for the following functions:-

$$(a) F = AB'CD + B'CD + ABC + B'C$$

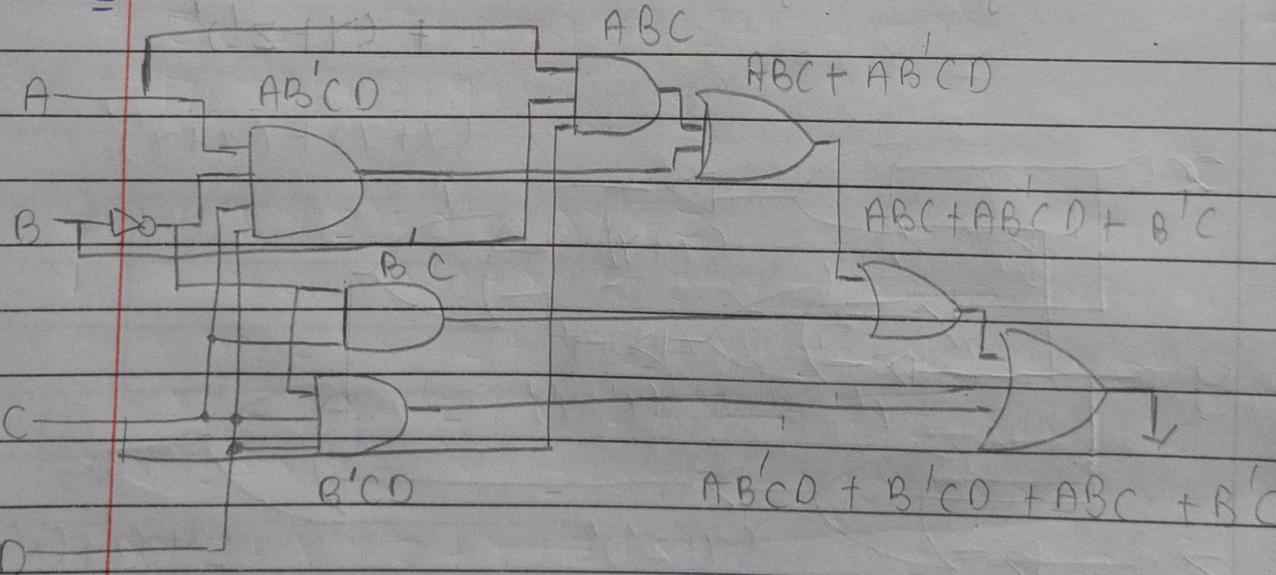


8908490CS048

(5)

$$(b) F = A'B'C + ABCE + AB'CD + A'B' + ABC$$

AB'CD

ABC'D + A'B'C + ABCE

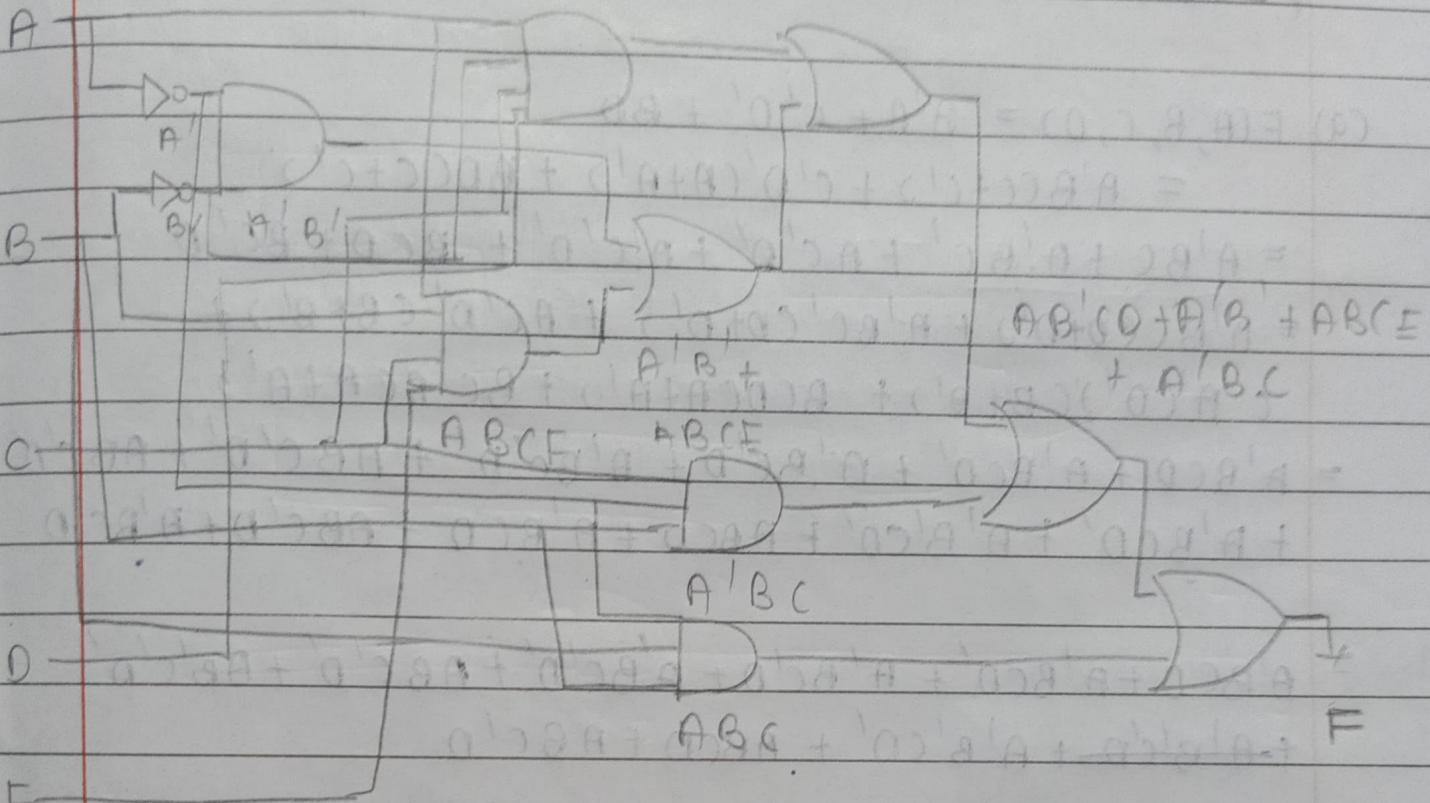

$$(S_1 + S_2 + S_3 + S_4 + S_5 + S_6 + S_7 + S_8 + S_9 + S_{10}) \oplus$$

$$(S_1 + S_2 + S_3 + S_4 + S_5 + S_6 + S_7 + S_8 + S_9 + S_{10}) \oplus$$

$$(P_1 + P_2 + P_3 + P_4 + P_5 + P_6 + P_7 + P_8 + P_9 + P_{10}) \oplus$$

$$(S_1 + S_2 + S_3 + S_4 + S_5 + S_6 + S_7 + S_8 + S_9 + S_{10}) \oplus$$

19DCS098 (6)

Q- (5) Express the functions in sum of minterms and product of maxterms

$$\begin{aligned}
 (a) F(A, B, C, D) &= A'B + C'D' + BD \\
 &= A'BC(C+D') + C'D'(A+A') + BDCC+C'D \\
 &= A'BC + A'BC' + AC'D' + A'C'D' + BCD + BC'D \\
 &= A'BC(CD+D') + A'BC'(CD+D') + AC'D'(CB+B') + \\
 &\quad C'A'C'D'(CB+B') + BCD(A+A') + BC'D(A+A') \\
 &= A'BCD + A'BCD' + A'BC'D + A'BC'D' + ABC'D' + ABC'D \\
 &\quad + A'BCD' + A'BC'D' + ABCD + A'BCD + ABC'D + A'BC'D \\
 &= A'BCD + A'BCD' + A'BC'D + A'BC'D' + ABCD' + AB'C'D' \\
 &\quad + A'B'C'D + A'B'C'D' + ABCD + ABCD' \\
 &= \sum(M_5 + M_6 + M_7 + M_8 + M_9 + M_{10} + M_{11} + M_{12} + M_{13}) \\
 &= \sum(2 + 4 + 5 + 6 + 7 + 8 + 12 + 13 + 15) \\
 &= \prod(D + I + 3 + 9 + 10 + 11 + 14)
 \end{aligned}$$

$$\begin{aligned}
 (b) F(X, Y, Z) &= Y'Z + XY' + Z' \\
 &= Y'Z(X+X') + XY'(Z+Z') + Z'(X+X')(Y+Y') \\
 &= XY'Z + X'Y'Z + XY'Z + XY'Z' + YZ' + Y'Z' \\
 &= XY'Z + X'Y'Z + XY'Z + XY'Z' + YZ'(X+X') + YZ'(X+X') \\
 &= XY'Z + X'Y'Z + XY'Z + XY'Z' + XYZ' + X'YZ' + XY'Z' + X'Y'Z' \\
 &= XY'Z + X'Y'Z + XY'Z + XY'Z' + XYZ' + XYZ' + XY'Z' + X'Y'Z' \\
 &= \sum(5 + 1 + 4 + 6 + 2 + 0) \\
 &= \sum(0 + 1 + 2 + 4 + 5 + 6) \\
 &= \prod(3 + 7)
 \end{aligned}$$

19DC8048

7

$$\begin{aligned}
 (c) F(A, B, C, D) &= (A' + B)CB'C + C \\
 &= A'B' + A'C + BB' + BC \\
 &= A'B'C + A'B'C' + A'BC + A'B'C + ABC + A'BC \\
 &= ABC + A'BC + A'B'C + A'B'C' \\
 &= \sum(7+3+1+0) \\
 &= \sum(0+1+3+7) \\
 &= \prod(2+4+5+6)
 \end{aligned}$$

$$\begin{aligned}
 (d) F(w, x, y, z) &= (Y+Z)(X'+Y')(X'+Z) \\
 &= (Y+Z)(X'x' + X'z + X'y' + Y'z) \\
 &= X'y + X'y'z + X'y'y + Yy'z + X'z + X'z + X'y'z \\
 &= X'y + X'y'z + X'z + X'y'z + Y'z \\
 &= X'y(z+z') + X'y'z + Y'z(Y+Y') + X'y'z + Y'z(X+x') \\
 &= X'y'z + X'y'z' + X'y'z + X'y'z + X'y'z + X'y'z + X'y'z + X'y'z \\
 &= X'y'z + X'y'z' + X'y'z + X'y'z \\
 &= \sum(3+2+1+5) \\
 &= \sum(1+2+3+5) \\
 &= \prod(0+4+6+7)
 \end{aligned}$$

\* Define:-

(i) Fanout - Specifies the number of standard loads that output of a gate can drive without impairing its normal operation

(ii) Power Dissipation -  $I_f$  is the supplied power required to operate the gate.  $I_f$  represents the power delivered to gate from supply

19DCS098

(8)

(iii) Propagation Delay - It is the average transition delay time for a signal to propagate from input to output when binary signals change in value.

(iv) Noise Margin - It is the maximum noise voltage added to input signal of digital circuit that does not cause an undesirable change in circuit output.

$$(S + I)x(S + R + K)(S + R) = (S + R)(S + R) = (R)$$

$$(S'R + I'x + S'Rx + I'x' + R'x)(S + R) =$$

$$S'R +$$

$$S'R + S'Rx + S'Rx + S'R'x + R'x =$$

$$(I'x + x)S'R + S'Rx + I'x + R'x =$$

$$I'x + S'R'x + S'Rx + S'R'x + S'Rx + S'R'x + S'R'x + S'R'x =$$

$$4S'R'x + S'Rx + S'R'x + S'R'x =$$

$$(2^2 + 1 + 2 + 2)S =$$

$$(2 + 2 + 2 + 1)S =$$

$$(2 + 2 + 1 + 1)S =$$

Block 10 notes for column 9NT 29/12/2023 - lesson 11  
skipped over step 10 to the two final sections lesson 11 efficiency function