

Seat no. _____

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Third semester of B. Tech (IT) Examination

March-April 2018

IT241 Digital Electronics

Date: 30.03.2018, Friday

Time: 1.30 p.m. To 04.30 p.m.

Maximum Marks: 70

Instructions:

1. The question paper comprises two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION I

Q - 1 Do as directed.

[8]

- 1) Given function $F = A \oplus B' \oplus C \oplus D' \oplus E'$ is equivalent to Ex-NOR function. State **TRUE** or **FALSE**
- 2) Write Dual of boolean equation: $X + XY = X$
- 3) Boolean equation $AB(A+B) = \underline{\hspace{2cm}}$
- 4) If boolean function $X \oplus Y = 1$ and $Y = 1$ then what is the value of X ?
- 5) Which one of the following is universal gate?
 - a) Ex-OR gate
 - b) AND gate
 - c) NAND gate
 - d) NOT gate
- 6) How many inputs does a full subtractor has?
 - a) 1
 - b) 2
 - c) 3
 - d) 4
- 7) In a multiplexer the output depends on its
 - a) Data inputs
 - b) Select inputs
 - c) Select outputs
 - d) None of the Mentioned
- 8) Ex-OR operation is associative. State **TRUE** or **FALSE**.

[12]

Q - 2 Do as directed. (Any Three)

- 1) Implement ex-or function using NAND gates only. Draw circuit diagram of the same.
- 2) Discuss design procedure of full adder circuit in detail. Also draw neat and clean logic diagram of the same.
- 3) Reduce boolean function $F = BC + AC' + AB + BCD$ to four literals.
- 4) Draw neat and clean logic diagram of 2 x 4 decoder.

Q - 3 Do as directed.

[15]

- 1) Design a combinational circuits to convert BCD code to Excess-3 code.
- 2) Simplify boolean function $F(A,B,C,D) = (m_0, m_2, m_5, m_6, m_8, m_{10})$ using K-Map.
- 3) Implement function $F(A,B,C) = (m_1, m_3, m_5, m_6)$ using multiplexer.

SECTION II

Q - 4 Do as directed.

[9]

- 1) Draw Block diagram of sequential circuit.
- 2) If Current state of a T-FlipFlop is 1 and input is 1 then next state will also be 1. State **TRUE** or **FALSE**.
- 3) Represent $(12)_{10}$ in excess-3 encoding.
- 4) Represent $(15)_{10}$ in BCD encoding.

- 5) If SR-FlipFlop is given then we can construct a D-FlipFlop by just adding one NOT gate to it. state **TRUE** or **FALSE**.
- 6) Draw state table of T-FlipFlop
- 7) Which input combination of SR-FlipFlop is invalid?
 - a) 00
 - b) 01
 - c) 10
 - d) 11
- 8) How is a J-K flip-flop made to toggle?
 - a) J=0, K=0
 - b) J=1, K=0
 - c) J=0, K=1
 - d) J=1, K=1
- 9) How many flip-flops are required to make a MOD-32 binary counter?
 - a) 3
 - b) 4
 - c) 5
 - d) 6

Q - 5 Do as directed. (Any three)


[12]

- 1) Discuss design procedure of SR-FlipFlop in detail. Also draw digital circuit of same. Why one of its input combinations are not valid?
- 2) $M=(1010100)_2$ and $N=(1000100)_2$. Perform $M - N$ with 2's complement representation.
- 3) What is Asynchronous and synchronous sequential circuits?
- 4) Draw logic diagram of Johnson counter.

Q - 6 Do as directed.(Any two)

[14]

 - 1) For given state diagram, find equivalent state diagram with minimal states.



- 2) Explain design procedure of binary up counter to count sequence 0 to 3. Also draw all necessary diagrams.
- 3) Draw a circuit of 4-bit registers with parallel load.
