

Practical No. 6


Aim: To implement full adder combinational circuit.

Apparatus: Logic Gate ICs, Connecting wires, Bread Board, Power supply, LED, DMM.

Theory:

Full adder is developed to overcome the drawback of Half Adder circuit. It can add two one-bit numbers A and B, and carry c . The full adder is a three input and two output combinational circuit.


BLOCK DIAGRAM:

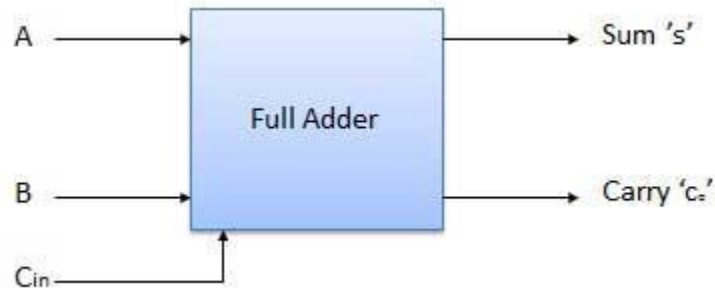

TRUTH TABLE:

Inputs			Output	
A	B	C _{in}	S	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Combinational Logic:

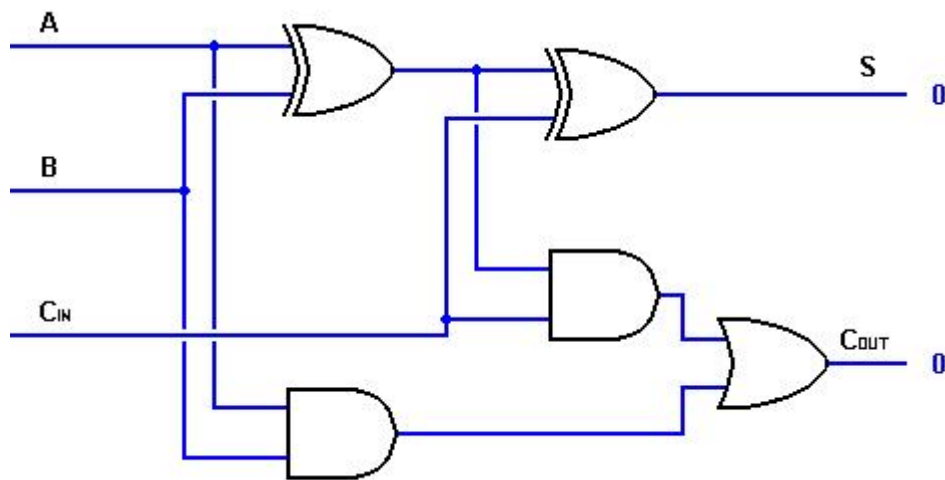


Procedure:

- i) Do the connection as per Combinational logic diagram for various input data.
- ii) Apply proper input condition and observe the output information of using DMM.
- iii) Compare theoretical data with observation and write conclusion.

Observation Table:

Tinker Cad Simulation:

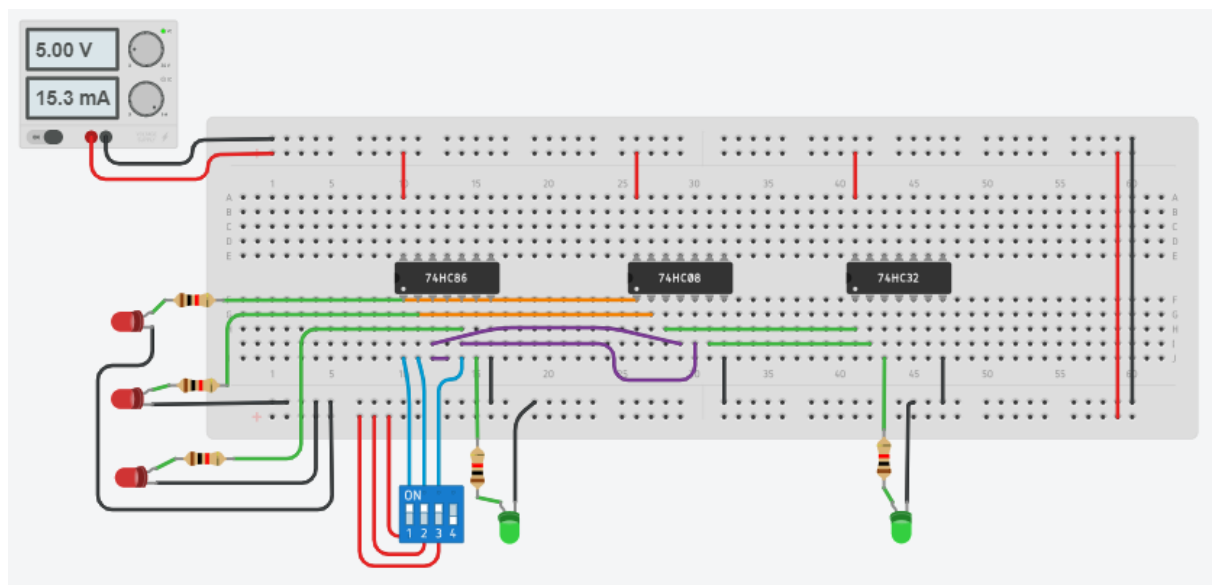

Observation Table:

Inputs			Outputs	
A	B	C	Sum (s)	Carry (c)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

CONCLUSION:

A full adder circuit is central to most digital circuits that perform addition or subtraction. It is so called because it adds together two binary digits, plus a carry-in digit to produce a sum and carry-out digit.