

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Third Semester of B. Tech. (CE/IT) Examination

November 2013

CE204 Digital Electronics

Date: 26.11.2013, Tuesday Time: 1.30p.m. To 4.30p.m. Maximum Marks: 70

Instructions:

1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.

SECTION-I

Q-1 Attempt the following.

- | | | |
|---|--|----|
| 1 | Convert $(0.513)_{10} = ()_8$ | 01 |
| 2 | Represent decimal number 8620 (a) in BCD (b) in Excess-3 code. | 01 |
| 3 | Find 10's Complement of $(935)_{11}$ | 01 |
| 4 | Using 2's complement perform $(1010100)_2 - (1000100)_2$ | 02 |
| 5 | Convert hexadecimal 2AC5D to decimal and octal. | 02 |

- Q-2(a) Design Full Adder with two half adder and an OR gate. 04
- (b) Write a short note on Johnson counter with timing sequence. 04
- (c) Find the complement of the following Boolean function and reduce them to minimum number of literals. 06
- (i) $F = (BC' + A'D)(AB' + CD')$ (ii) $F = [(AB)'A][(AB)'B]$

OR

- Q-2 (a) Design a combinational circuit with four input lines that represent decimal digit in BCD and four output lines that generate the 9's complement of input digit. 06
- (b) Design a combinational circuit to check for odd parity of 3 bits. 04
- (c) Explain the operation of RS flipflop along with its symbol, characteristic table and characteristic equation. 04

- Q-3(a) Determine the prime implicants of the function 06
- $F(w, x, y, z) = \sum m(1, 4, 6, 7, 8, 9, 10, 11, 15)$
- (b) Draw and Explain 4-bit binary ripple counter with JK flipflop. 04
- (c) (i) Implement the Boolean function: 04
- $F = AB'CD' + A'BCD' + AB'CD + A'BC'D$ with EX-OR & AND gate.
- (ii) Show that $A \oplus B \oplus C \oplus D = \sum m(0, 3, 5, 6, 9, 10, 12, 15)$

OR

- Q-3 (a) Explain serial transfer operation from register A to register B. 04
- (b) Implement full adder with a decoder and two OR gate. 04

- (c) Built the following function in SOP and POS form using kmap. 06
 $F(A,B,C,D) = \sum m(0,1,2,5,8,9,10)$

SECTION II

Q-4 Do as directed.

- 1 Design 4x16 decoder with two 3x8 decoder. 02
- 2 What is the difference between synchronous and ripple counter. 02
- 3 Draw the logic diagram of 2 to 4 line decoder with enable(E) input 01
- 4 Show that the dual of the Exclusive-OR is equal to its complement. 02

Q-5 (a) Design a counter with the sequence 0,1,2,4,5,6 and repeat. Use J-K flip-flop. 05

(b) Implement given function with multiplexer: $F(A,B,C,D) = \sum m(0,1,3,4,8,9,15)$. 04

(c) Write a short note on magnitude comparator with necessary diagrams. 05

OR


Q-5 (a) A combinational circuit is defined by the functions: 05

$$F_1(A,B,C) = \sum(0,1,2,4)$$

$$F_2(A,B,C) = \sum(0,5,6,7)$$

Implement the boolean equation with PLA.

 
(b) Design a clocked sequential circuit whose state diagram is given below. The type of flipflop to be used is JK. 07



(c) Define: Propagation delay, Power dissipation. 02

Q-6 (a) Design Mod-6 counter using T- flip flop. 06

 - (b) Give the logic implementation of 32x4 ROM using a decoder of suitable size. 04
size.
- (c) Draw state table for the following state diagram and reduce it to possible number of states and redraw the state diagram. 04



OR

- Q-6(a) Reduce the following function using kmap and implement it with NAND gates. 05

$$F(a,b,c,d) = \sum m(0,1,2,3,5,7,8,9,10,12,13)$$
- (b) Implement EX-NOR gate using NAND and NOR gate. 05
- (c) i) The content of 4 bit shift register is initially 1101. The register is shifted 4 times to right; with the serial input 101101. What is the content of the register after each shift? 04
 ii) What is the difference between serial and parallel transfer?